



UM EECS 270 F22

Introduction to Logic Design

8. Combinational Building Blocks

Combinational Blocks



- Goal is to create a “toolbox” of devices that are frequently required in logic design
 - Originally, each device would be on its own IC
 - Today, circuit can be made so small that many circuits can fit on a single chip
 - VLSI can *instantiate* adders, comparators, etc., as many times as needed within a larger circuit
 - We would like to identify other frequently used combinational circuits and find small circuits for them in advance

Equality Comparator



- Want a signal, EQ, that is 1 iff two 4-bit numbers A and B, are equal. Under what logic conditions are A and B equal?
 - Equal if $a_3 = b_3$ AND $a_2 = b_2$ AND $a_1 = b_1$ AND $a_0 = b_0$
- Which gate performs an equality comparison?
 - XNOR!

A	B	$A \odot B$
0	0	1
0	1	0
1	0	0
1	1	1

$$EQ = (a_3 \odot b_3) \cdot (a_2 \odot b_2) \cdot (a_1 \odot b_1) \cdot (a_0 \odot b_0)$$




How many gates are required to implement an n -bit “parallel” comparator?

Assume $n = 2^k$

$$\begin{aligned}
 \# \text{gates} &= 2^k + 2^{k-1} + 2^{k-1} + \dots + 2^0 \\
 &= 2^{k+1} - 1 \\
 &= 2n - 1
 \end{aligned}$$


A “Series” Comparator Implementation

 

How many gates are required to implement an n -bit comparator?

- Comparing first two bits
- Comparing each bit: 2 gates
- After comparing first 2 bits, there are $n-2$ bits left to compare for a total of $2(n-2)$ gates
- Total number of gates required: $2(n-2) + 3 = 2n - 1$
- “Series” and “parallel” implementations require the same number of gates! Is there a reason to prefer one implementation over the other?

Magnitude Comparator

 


- Want to design a signal, $AgrB$, that is 1 if $A > B$ (A and B are 4-bit numbers). Under what conditions is $A > B$?
 - $A > B$ if $a_3 = 1$ and $b_3 = 0$
 - $A > B$ if $a_2 = 1$ and $b_2 = 0$ and $a_3 = b_3$
 - $A > B$ if $a_1 = 1$ and $b_1 = 0$ and $a_2 = b_2$ and $a_3 = b_3$
 - $A > B$ if $a_0 = 1$ and $b_0 = 0$ and $a_1 = b_1$ and $a_2 = b_2$ and $a_3 = b_3$

$AgrB$


$$\begin{aligned}
 & (a_3 \odot b_3) \cdot a_2 \cdot \overline{b_2} + \\
 & (a_3 \odot b_3) \cdot (a_2 \odot b_2) \cdot a_1 \cdot \overline{b_1} + \\
 & (a_3 \odot b_3) \cdot (a_2 \odot b_2) \cdot (a_1 \odot b_1) \cdot a_0 \cdot \overline{b_0}
 \end{aligned}$$

Decoder Circuit

 

Symbol:


2-to-4
Decoder

 

Cascading Decoders




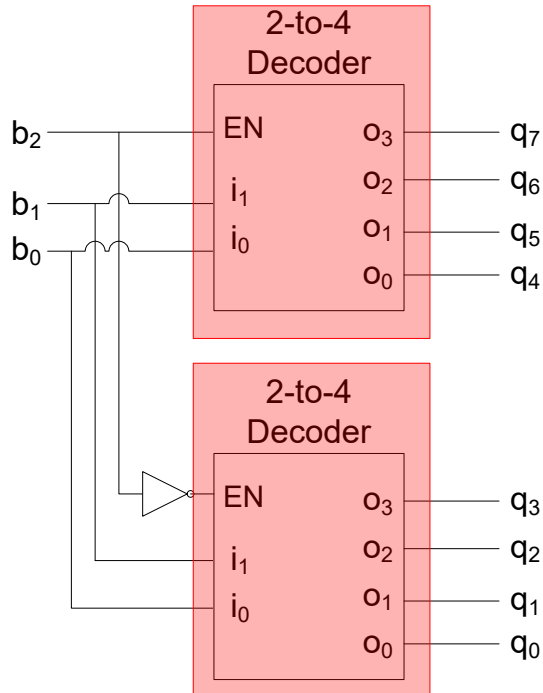Creating a 3-to-8 decoder from two 2-to-4 decoders:



b_2	b_1	b_0	
0	x	x	→ assert q_3 - q_0
1	x	x	→ assert q_7 - q_4

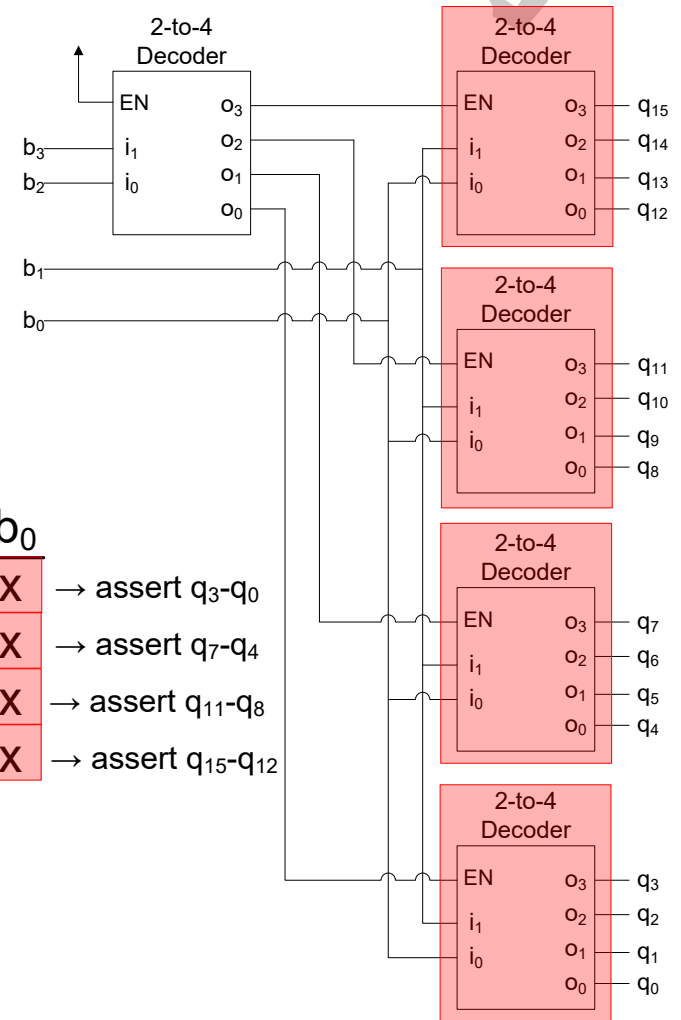Creating a 4-to-16 decoder from five 2-to-4 decoders:




b_3	b_2	b_1	b_0	
0	0	x	x	→ assert q_3 - q_0
0	1	x	x	→ assert q_7 - q_4
1	0	x	x	→ assert q_{11} - q_8
1	1	x	x	→ assert q_{15} - q_{12}

Implementing Functions with Decoders

- Any n-variable function can be implemented with a n-to- 2^n decoder!
 - Recall that each decoder output is implemented as a minterm of the input variables
 - Recall that any function can be implemented as a sum of minterms
 - Therefore, any function can be implemented as a sum of decoder outputs!


$$F = \sum_{X,Y,Z} (0,2,4,5)$$

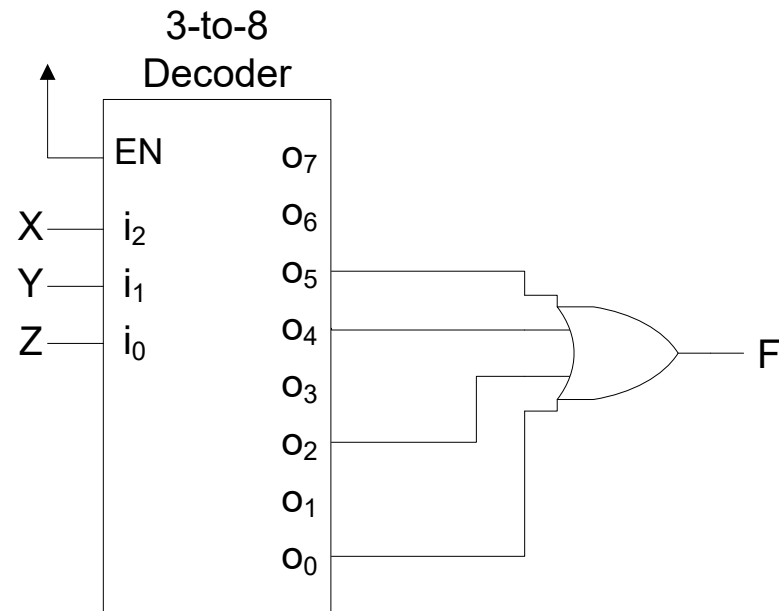

Encoders



- Opposite of decoders: an encoder takes as input a code with a large number of bits and outputs a corresponding code with a small number of bits
- Most common encoder maps a 2^n one-hot code to an n -bit binary number, where the binary number represents the input number that is asserted
- What if all input signals are deasserted? Requires additional output, usually called A (active) that is asserted if *at least* one input is asserted

 


i_3	i_2	i_1	i_0	o_1	o_0	A
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	1
0	1	0	0	1	0	1
1	0	0	0	1	1	1
all others				d	d	d

$$o_1 = i_3 + i_2$$

$$o_0 = i_3 + i_1$$


$$A = i_3 + i_2 + i_1 + i_0$$

 

- What if we want to allow *multiple* inputs to be asserted simultaneously and output the asserted input number with the highest priority?
 - This task is performed by a **priority encoder**

i_3	i_2	i_1	i_0	o_1	o_0	A
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

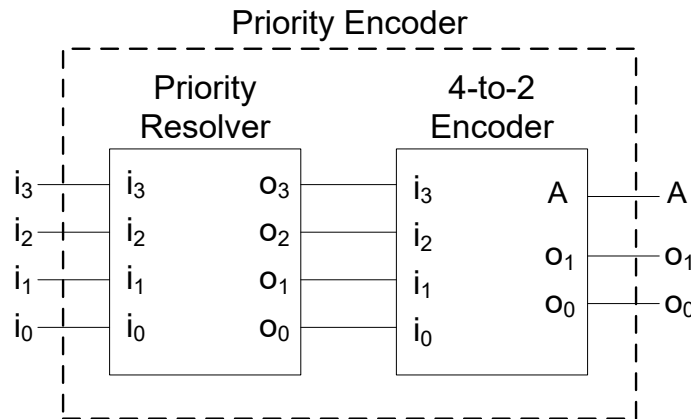- An easy way to implement: use our existing “toolbox” – specifically, make use of the encoder that we’ve already designed
- Need to add a circuit that will resolve priority: assert output signal corresponding to asserted input with highest priority



i_3	i_2	i_1	i_0	o_3	o_2	o_1	o_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	x	0	0	1	0
0	1	x	x	0	1	0	0
1	x	x	x	1	0	0	0

$$o_3 = i_3$$

$$o_2 = i_2 \cdot \overline{i_3}$$

$$o_1 = i_1 \cdot \overline{i_2} \cdot \overline{i_3}$$





$$o_0 = i_0 \cdot \overline{i_1} \cdot \overline{i_2} \cdot \overline{i_3}$$

Multiplexer (Mux)

- A **mux** is a digital switch
- The output copies one of n data inputs, depending on the value of the *select inputs*
- Implementation:

$$q = s'_1 s'_0 d_0 + s'_1 s_0 d_1 + s_1 s'_0 d_2 + s_1 s_0 d_3$$

Product terms are mutually exclusive!

    

Building large multiplexers from smaller multiplexers (and other blocks)

...using four 4-input muxes and 1 2-to-4 decoder


S ₃	S ₂	S ₁	S ₀
0	0	X	X
0	1	X	X
1	0	X	X
1	1	X	X

→ select d₃-d₀

→ select d₇-d₄

→ select d₁₁-d₈

→ select d₁₅-d₁₂

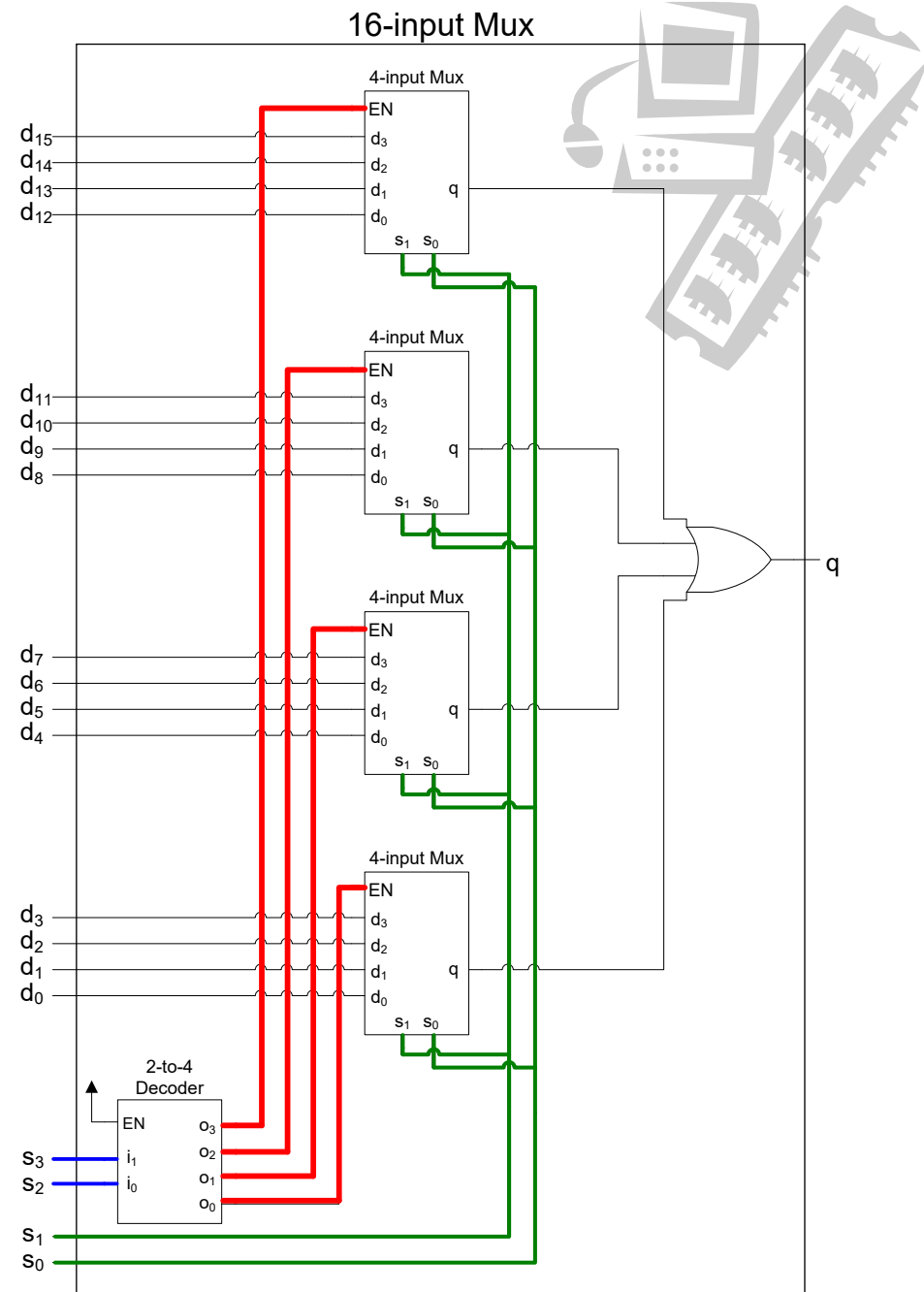

...using five 4-input muxes


S_3	S_2	S_1	S_0
0	0	x	x
0	1	x	x
1	0	x	x
1	1	x	x

→ select d_3 - d_0

→ select d_7 - d_4

→ select d_{11} - d_8


→ select d_{15} - d_{12}

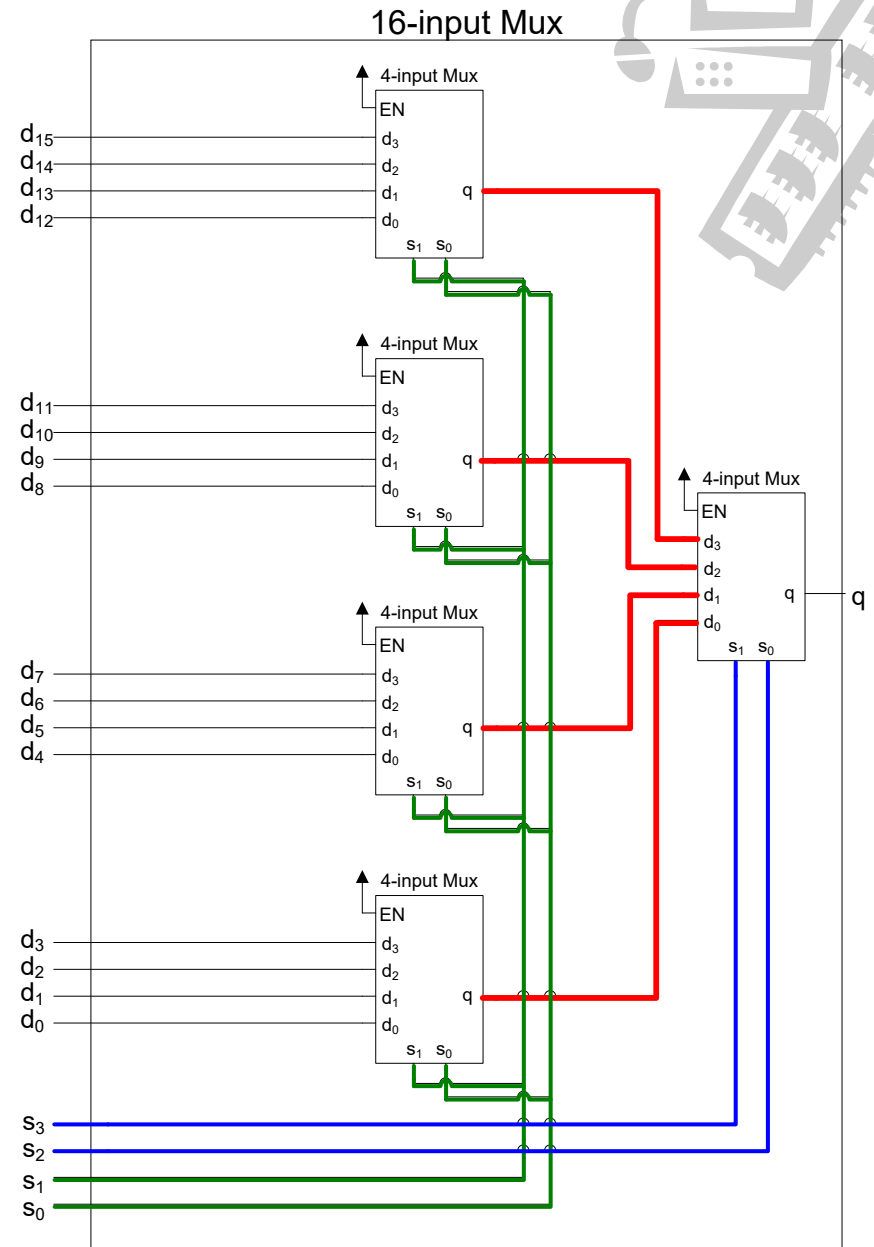

Implementing Functions With a Multiplexer


- We can implement an n -variable function using an n -select (2^n -input) mux

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

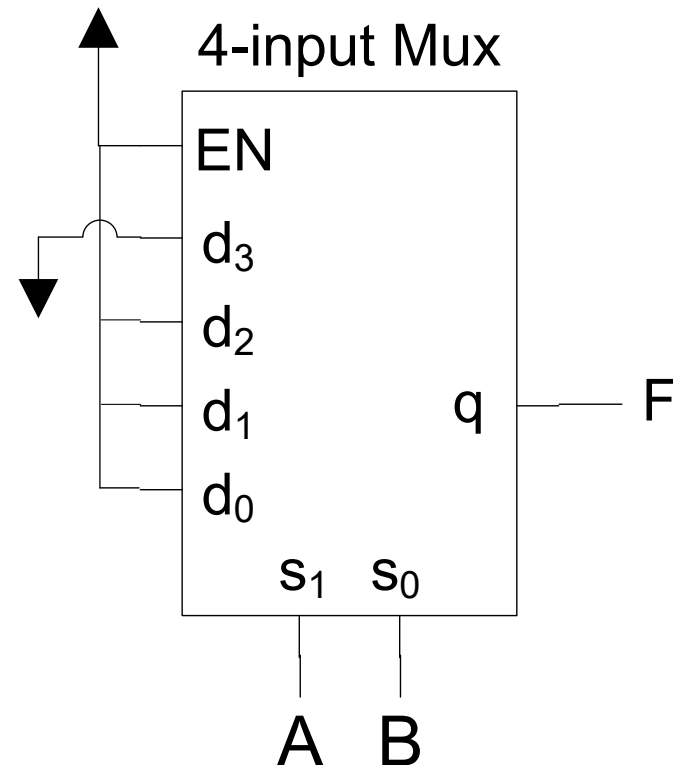

- We can do better: we can implement an n -input function with a 2^{n-1} -input mux!

A	B	C	F	
0	0	0	0] d_0
0	0	1	0	
0	1	0	1] d_1
0	1	1	1	
1	0	0	0] d_2
1	0	1	1	
1	1	0	1] d_3
1	1	1	0	

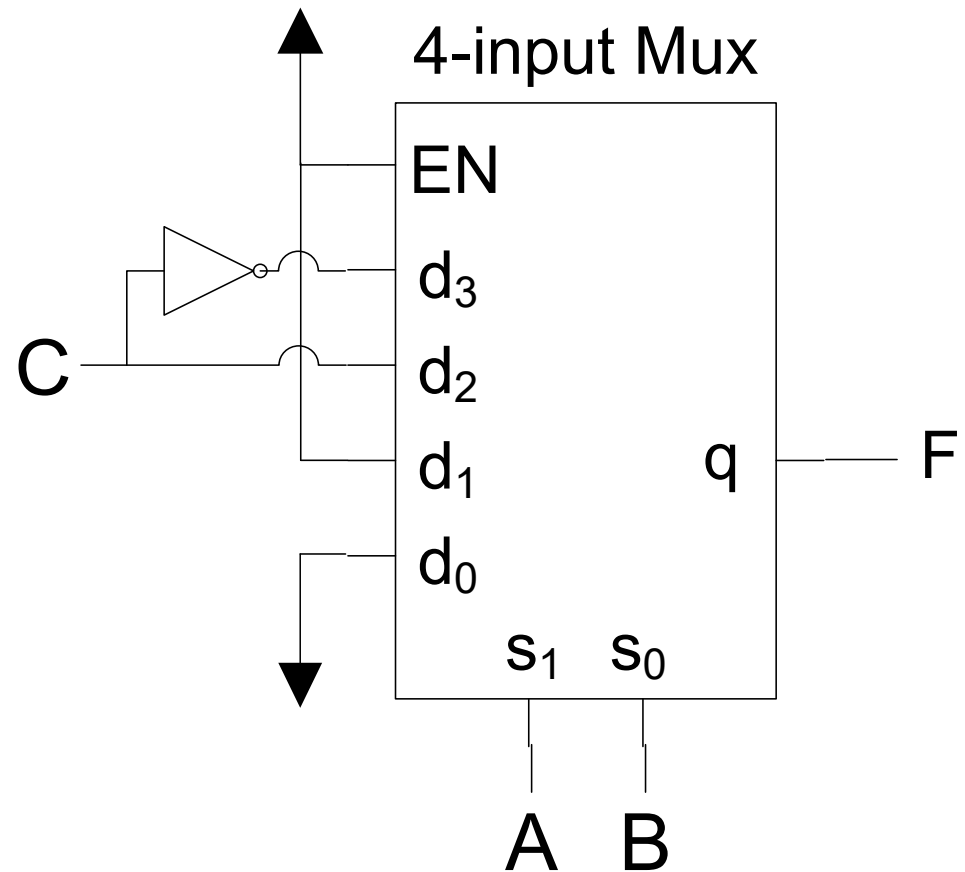


In Class Exercise



Implement the following 3-input function using a single 4-input mux:

$$F = \sum_{X,Y,Z} (0,3,4,5,6)$$

X	Y	Z	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

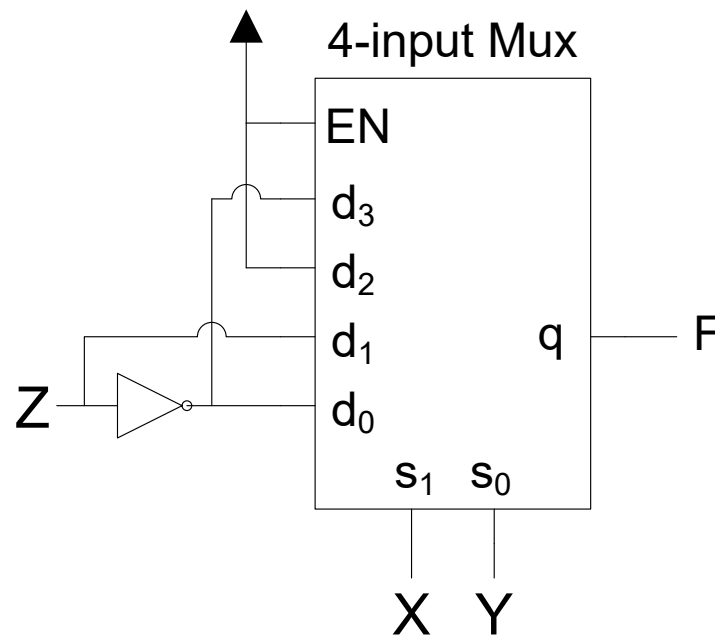

Function Implementation with MUX *is Application of* Boole/Shannon Expansion Theorem




$$F(W, X, Y, Z) = W'X'Z + XY'Z' + XYZ + WXY$$


$$= W'Z'(?) + W'Z(?) + WZ'(?) + WZ(?)$$

$$= W'Z'(XY') + W'Z(X' + XY) + WZ'(XY' + XY) + WZ(XY)$$

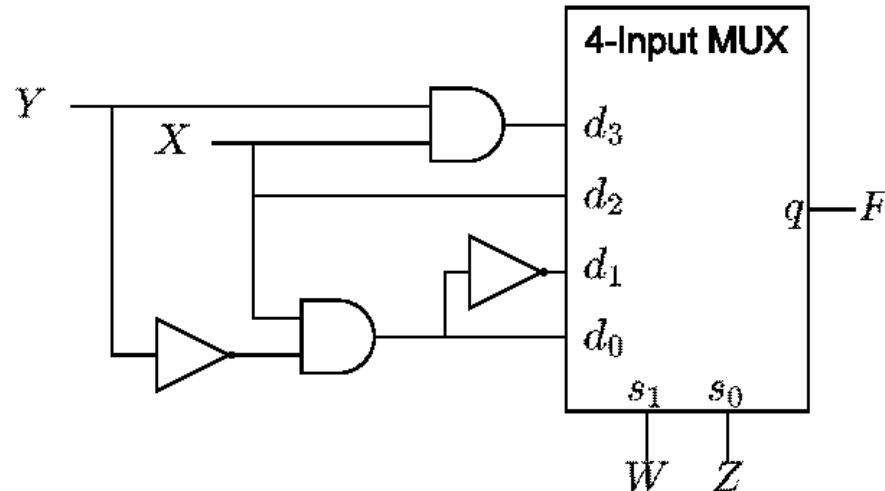
$$= W'Z'(XY') + W'Z(X' + Y) + WZ'(X) + WZ(XY)$$



Demultiplexer (demux)

 

 
- A **demux** connects an input signal to one of several output signals, depending on the value of the select signals




s_1	s_0	y_0	y_1	y_2	y_3
0	0	IN	0	0	0
0	1	0	IN	0	0
1	0	0	0	IN	0
1	1	0	0	0	IN

2-to-4 Decoder						
EN	i_1	i_0	O_0	O_1	O_2	O_3
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

 - How to implement?
 - TT should look very familiar...
 - Use a decoder!



Tri-State Gates

 


Tri-state Buffer

C	Q
0	High Impedance
1	D

→ D — • — • — Q


→ D ————— Q

Other tri-state devices:

 


Tri-state Inverter

C	Q
0	High Impedance
1	\bar{D}

 

Active low
Tri-state Buffer

C	Q
0	D
1	High Impedance


 


Active low
Tri-state Inverter

C	Q
0	\bar{D}
1	High Impedance

- Is it ok to connect the outputs of tri-state devices?
 - $C_1 = C_0 = 1$ and $D_1 \neq D_0 \rightarrow$ bad!
 - $C_1 = C_0 = 0 \rightarrow Q = ?$
 - $D_1 = D_0 \rightarrow$ OK!
- Typically, tri-state control signals are **one-hot**
 - Results in exactly one device connected to the output at a time
- Multiple devices can communicate over a single shared wire
 - Only one device is allowed to drive the wire at a time
 - A functional group of such wires is called a **bus**.

This looks familiar...

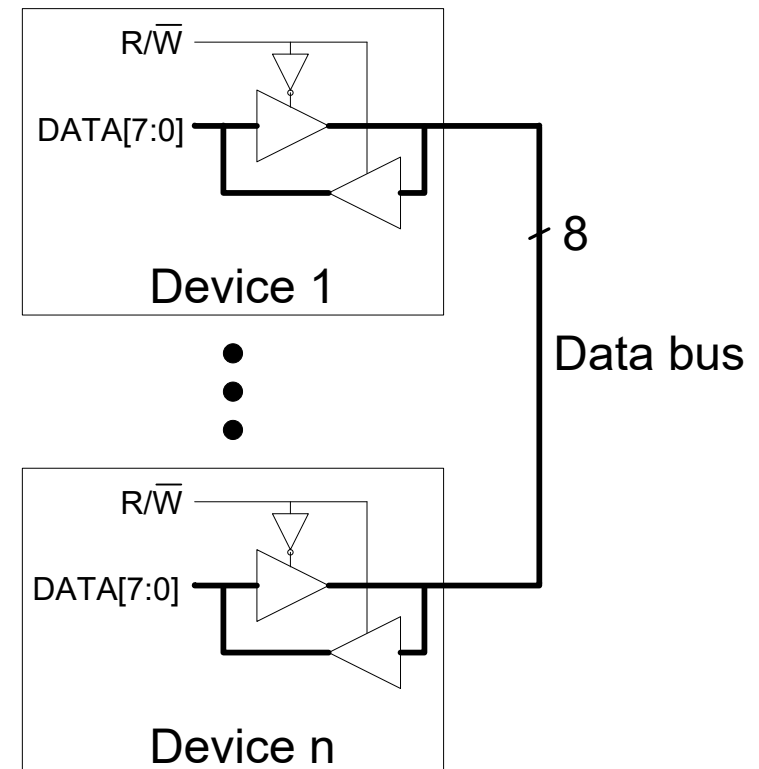 

Tying it all together...

